

ZX dictionary

CIRCUITS \longrightarrow ZX-diagrams

gate



diagr



Pauli Z = $\square{Z} = \square{Z[\pi]}$




Pauli X = $\square{X} = \square{X[\pi]}$

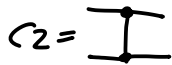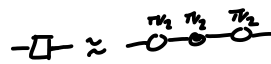


other stuff
(e.g. CZ, ToF, ...)



Ex

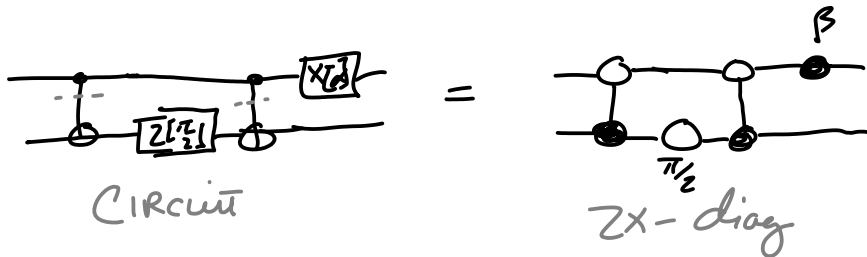

CNOT CIRCUITS & PHASE FREE ZX DIAGRAMS

CIRCUITS MADE JUST OUT OF  = 

ZX-DIAGS MADE OUT OF  AND 

PROP Any CNOT circuit is equal to a phase free ZX-diagram.



Q: What about the converse?

TODAY: (Unitary) phase-free ZX-diags \rightsquigarrow CNOT circuits.

$$\text{CNOT } |x, y\rangle \mapsto |x, x \oplus y\rangle$$

$$\text{CNOT } |x, y\rangle \mapsto |f_1(x, y), f_2(x, y)\rangle \quad \text{where } \begin{cases} f_1(x, y) = x \\ f_2(x, y) = x \oplus y \end{cases}$$

Def A function of the form $f(x_1, \dots, x_n) = x_{i_1} \oplus \dots \oplus x_{i_k}$ is called a parity map.

Parities.

Def The field \mathbb{F}_2 has elements $\{0, 1\}$ where:

$$x \cdot y := x \wedge y \quad x + y = x \oplus y \quad (\text{ie. } x + y \text{ mod } 2)$$

Sometimes we call some $x \in \mathbb{F}_2$ a parity.

$$\text{par}(\vec{b}) = \sum_i b_i$$

in \mathbb{F}_2

$\text{par}(\vec{b}) = 0$ means \vec{b} has an even # of 1's
 $\text{par}(\vec{b}) = 1$ means odd #.

Parities for subsets of bits:

$$(1 \ 0 \ 1 \ 1) \begin{pmatrix} b_1 \\ b_2 \\ b_3 \\ b_4 \end{pmatrix} = b_1 \oplus b_3 \oplus b_4$$

Multiple parities at once:


$$\underbrace{\begin{pmatrix} 1 & 0 & 1 & 1 \\ 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 \end{pmatrix}}_{\text{parity matrix.}} \begin{pmatrix} b_1 \\ b_2 \\ b_3 \\ b_4 \end{pmatrix} = \begin{pmatrix} b_1 \oplus b_3 \oplus b_4 \\ b_2 \oplus b_3 \\ b_1 \oplus b_4 \\ b_4 \end{pmatrix}$$

Thm The action of a CNOT circuit on basis elements is defined by an invertible parity matrix:

$$C|b_1, \dots, b_n\rangle = |c_1, \dots, c_n\rangle$$

where
$$P \begin{pmatrix} b_1 \\ \vdots \\ b_n \end{pmatrix} = \begin{pmatrix} c_1 \\ \vdots \\ c_n \end{pmatrix}.$$


e.g.

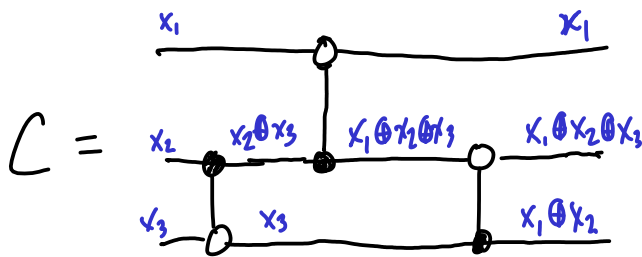

$$C|x_1, x_2, x_3\rangle = |x_1, x_1 \oplus x_2 \oplus x_3, x_1 \oplus x_2\rangle$$


$$\underbrace{\begin{pmatrix} 1 & 0 & 0 \\ 1 & 1 & 1 \\ 1 & 1 & 0 \end{pmatrix}}_P \begin{pmatrix} x_1 \\ x_2 \\ x_3 \end{pmatrix} = \begin{pmatrix} x_1 \\ x_1 \oplus x_2 \oplus x_3 \\ x_1 \oplus x_2 \end{pmatrix}$$

Special case: Single CNOT.

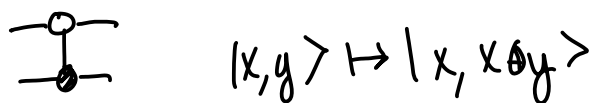

$$\underbrace{\begin{pmatrix} 1 & 0 \\ 1 & 1 \end{pmatrix}}_P \begin{pmatrix} x \\ y \end{pmatrix} = \begin{pmatrix} x \\ x \oplus y \end{pmatrix}$$

More generally:

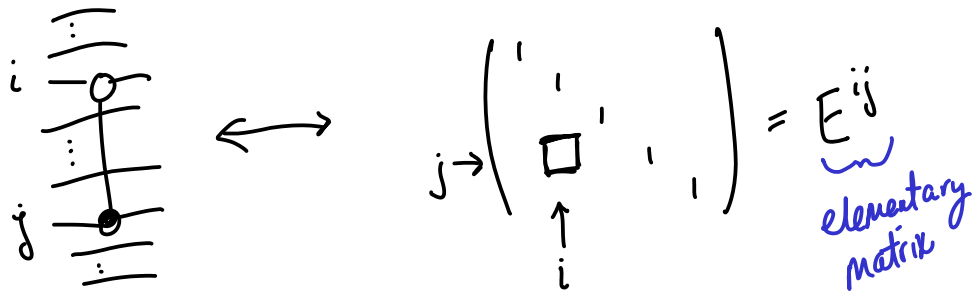

$$E^{ij}A = A'$$

↑
row $j = \text{row } j + \text{row } i$


$$A E^{ji} = A'$$

↑
col $j := \text{col } i + \text{col } j$

Suppose $P E^{ij} \dots E^{ik} = I$,


then $P = E^{ik} \dots E^{ij}$

↑ ↑ ↑
parity matrix CNOT gates!

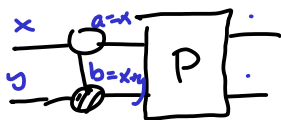

$$\begin{pmatrix} a & b \\ c & d \end{pmatrix} \begin{pmatrix} 1 & 0 \\ 1 & 1 \end{pmatrix} = \begin{pmatrix} a+b & b \\ c+d & d \end{pmatrix}$$

$$C_1 = C_1 + C_2$$

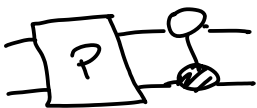


$$\begin{pmatrix} 1 & 0 \\ 1 & 1 \end{pmatrix} \begin{pmatrix} a & b \\ c & d \end{pmatrix} = \begin{pmatrix} a & b \\ a+c & b+d \end{pmatrix}$$

$$R_2 = R_2 + R_1$$


Algorithm: CNOT-SYNTH:

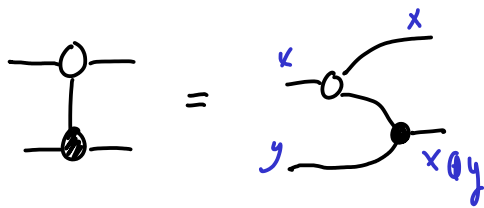- * Start w/ Parity matrix P , empty circ. C .
- * Do Gauss-Jordan reduction of columns of P .
 - Whenever an elem. col operation E^{ji} is applied, append $CNOT^{ji}$ to C .
- * C now implements P .



More general parity maps:

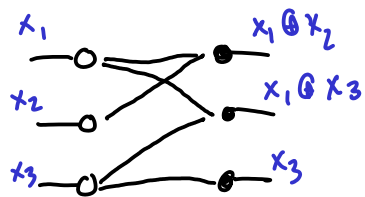
$$P = \begin{pmatrix} 1 & 1 & 0 \\ 1 & 0 & 1 \\ 0 & 0 & 1 \end{pmatrix} \begin{pmatrix} x_1 \\ x_2 \\ x_3 \end{pmatrix} = \begin{pmatrix} x_1 \otimes x_2 \\ x_1 \otimes x_3 \\ x_3 \end{pmatrix}$$




← implements P !

Lecture 10

Ex

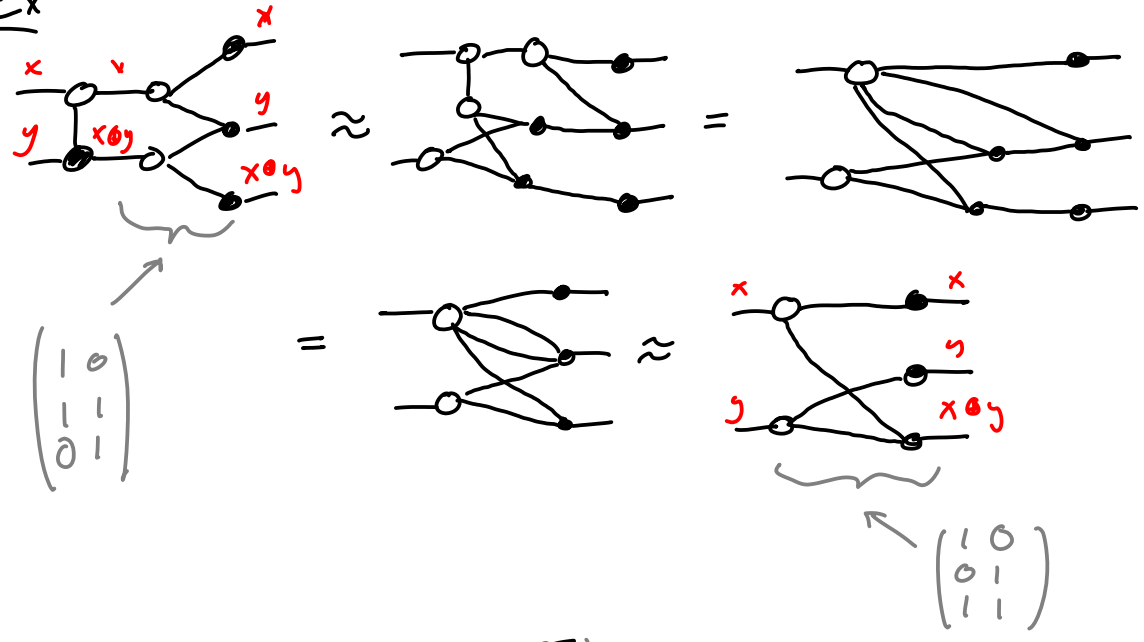


LEM 4.2.3

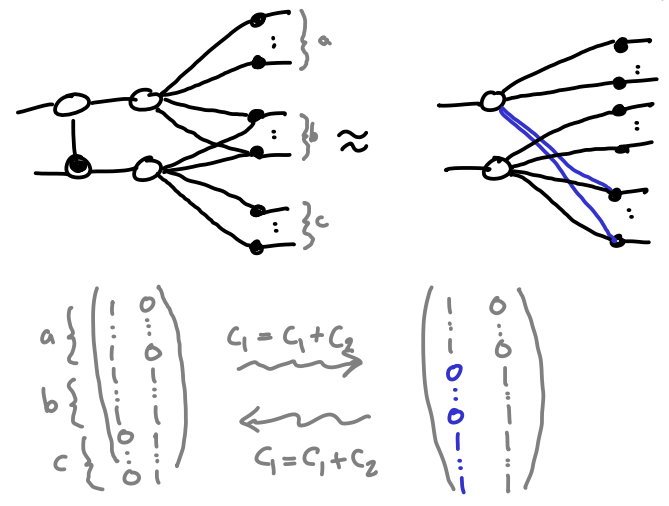

Ex
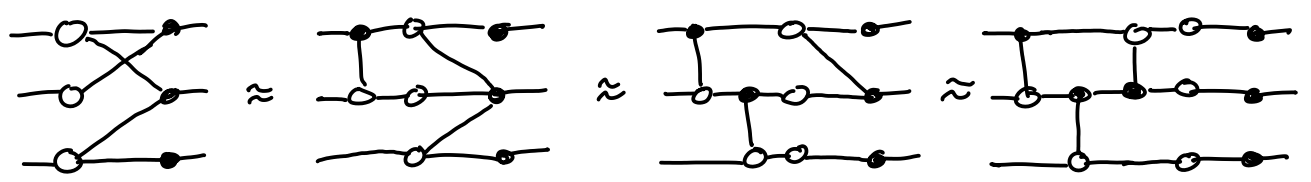
$$\begin{pmatrix} 1 & 1 & 0 \\ 1 & 0 & 1 \\ 0 & 0 & 1 \end{pmatrix} \xrightarrow{C_2 = C_2 + C_1} \begin{pmatrix} 1 & 0 & 0 \\ 1 & 1 & 1 \\ 0 & 0 & 1 \end{pmatrix} \xrightarrow{C_3 = C_3 + C_2} \begin{pmatrix} 1 & 0 & 0 \\ 1 & 1 & 0 \\ 0 & 0 & 1 \end{pmatrix} \xrightarrow{C_1 = C_1 + C_2} \begin{pmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{pmatrix}$$



Def A spider is called

- * an input spider if it is conn. to an input
- * an output spider if it is conn. to an output
- * an interior spider otherwise.

Def A phase-free ZX-diagram is in parity normal form

- every Z spider is conn. to exactly 1 input
- every X spider is conn. to exactly 1 output
- no wires between spiders of the same type
- no parallel wires




P parity matrix.

Def A ZX-diagram is called 2-coloured if there are no Z-Z edges, X-X edges, parallel edges or self-loops.

Def A phase-free ZX diag. is in generalised parity form if it is 2-coloured and:

1. every input is conn. to Z, output to X
2. every sp. is conn to at most 1 input/output
3. no scalar spiders
- * 4. no edges between interior spiders

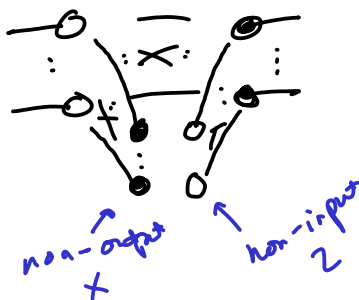

Algorithm 2: Reduction to generalised PNF.

1. apply (sp), (comp), and $0 = \bullet = 2$ as much as possible.
2. try to apply (sc) to a pair $0 \rightarrow \bullet$ where:
 - 0 is not an input
 - \bullet is not an output
3. if step 2 applied (sc), goto step 1. otherwise:
4. use (id) to make sure every input is conn. to Z & output conn. to X .


Thm Alg 2 terminates ^(sketch) in generalised PNF. _{efficiently}

Pf: Each iteration of steps 1-3 removes non-input Z spiders (and non-output X -spiders) without making new ones.


- \Rightarrow # iterations bounded by # of spiders
- after the loop, conds 3-5 are satisfied.
 - after step 4, conds 1-2 are satisfied. \square

Prop If D is unitary and in generalised PNF, then it is in PNF.

Pf If D has an interior X spider, then:

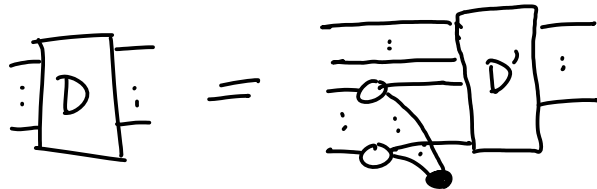

So:

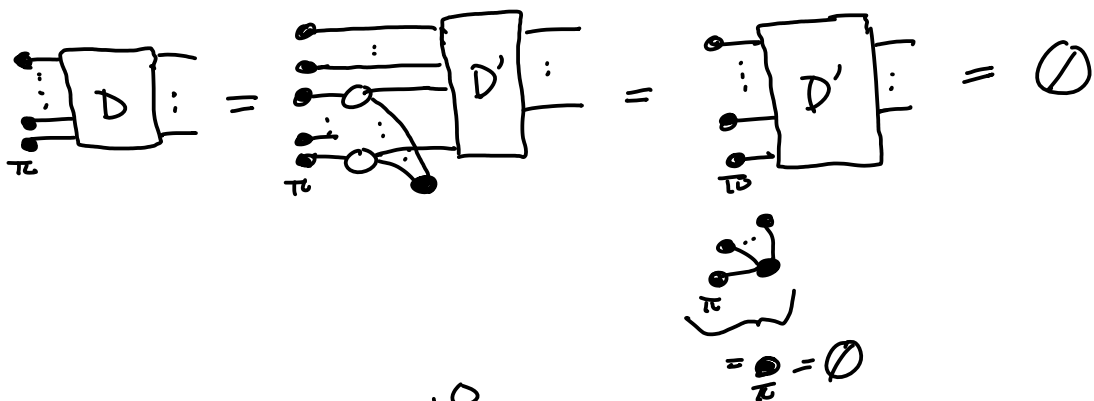

So, there exists $|\psi\rangle \neq 0$ st $D|\psi\rangle = 0$. But:

$$D^\dagger D|\psi\rangle = |\psi\rangle \neq 0. \quad \Downarrow$$

So D has no interior X -spiders. Similarly,

- D has no
- Z -sp's connected to >1 input
 - interior X sp's
 - X -sp's connected to >1 output.




Unitary \star
Phase-free \implies PNF \implies CNOT circuit.
 ZX

Clifford diagrams and circuits


Def A ZX-diagram is Clifford when it is made of Clifford spiders



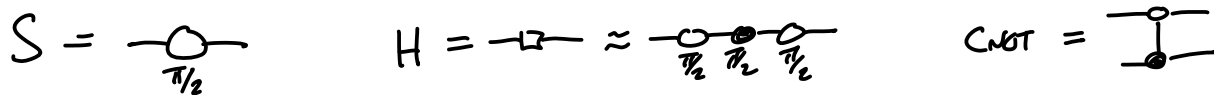Def Clifford circuits are circuits made from:



Ex Some common Clifford gates:

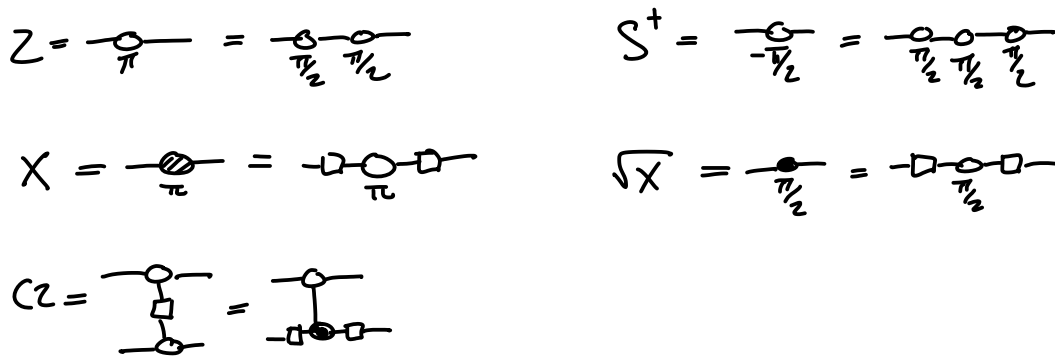

Ex Some non-Clifford gates:





Lecture 11

Def A Clifford state is a state $|\psi\rangle = C|0\dots 0\rangle$ for a Clifford circuit C .


Q: Why care about Cliffords?

* Contains useful states, e.g.

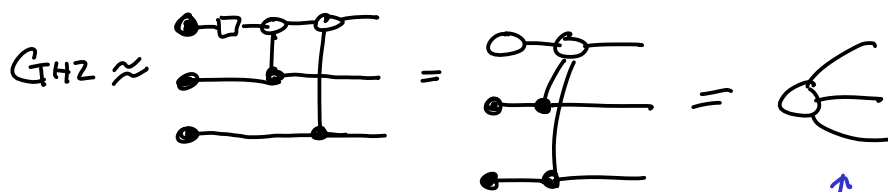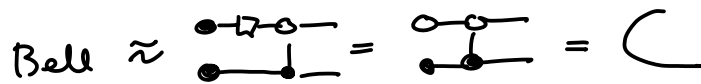

\uparrow
g. nonlocality in PQP

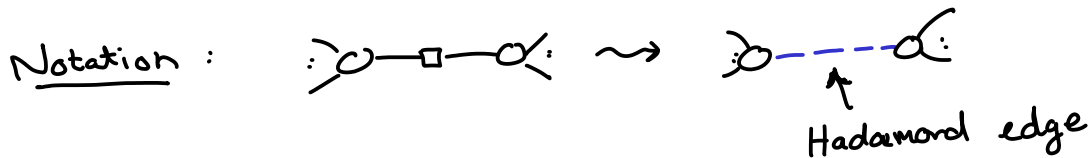- * Quantum error correction (later)
- * Eff. classical simulation (soon)
- * Rich rewrite theory (now!)



Def A ZX diagram is graph like if:

1. all spiders are Z spiders
2. all edges btw spiders are Hadamard edges
3. no parallel edges or self-loops
4. every input/output is connected to a spider.

Prop Every ZX-diagram is equal to a graph-like one.

Pf 1. Use $\text{X} \stackrel{cc}{=} \text{O}$ to elim X spiders.

• use $\text{H} \stackrel{hh}{=} \text{---}$ to cancel extra H's.

2. Use (sp) to elim non-H edges: $\text{O}_\alpha \text{---} \text{O}_\beta = \text{O}_{\alpha+\beta}$

3. For parallel H-edges:



For self-loops: $\text{O}_\alpha \stackrel{sp}{=} \text{O}_\alpha$




4. Use $\text{---} \stackrel{id}{=} \text{---} \text{O}$ if necessary.

e.g. $\text{---} = \text{---} \text{O} \leftarrow \text{g.l.}$





Ex

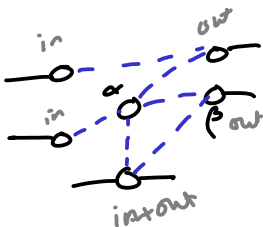



Def A graph-like diagram is called a graph state if:

- no inputs
- no interior spiders
- no phases

Ex

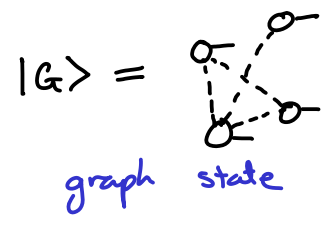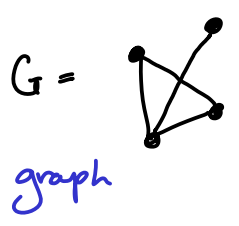

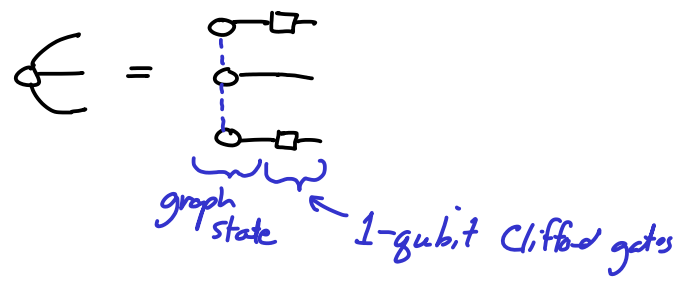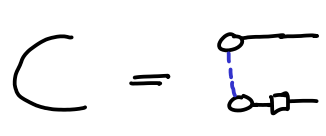Some states are almost graph states, e.g.




Def A graph state with local Cliffords (GSLC) is a state of the form $(U_1 \otimes \dots \otimes U_n) |G\rangle$ for some graph state $|G\rangle$ and 1-qubit Clifford gates U_i .

Thm Any Clifford state is = to a GSLC.

We'll need some new tools to prove this!

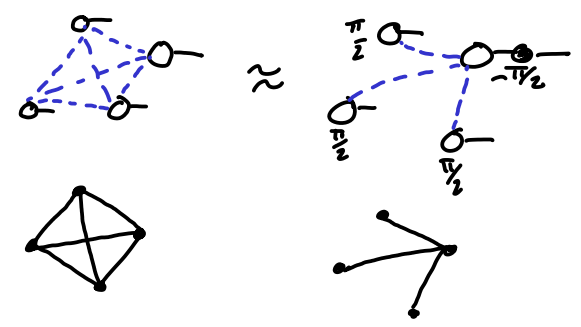First, note that for GSLCs, the graph can be deceiving!









Def Let $G=(V,E)$ be a graph and $u \in V$.


The Local complementation of G about u is a new graph $G * u = (V, E')$ where

$$\forall v, w \in N_G(u) \quad (v, w) \in E' \iff (v, w) \notin E.$$


\uparrow
 neighbourhood

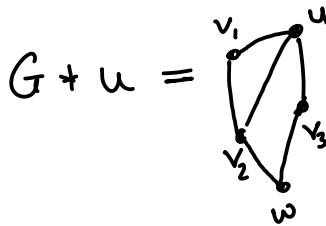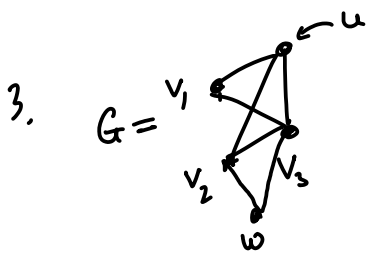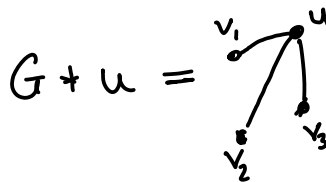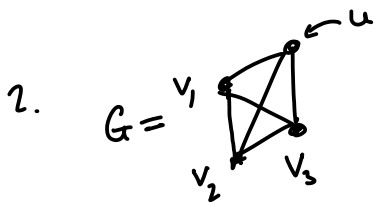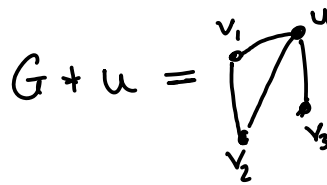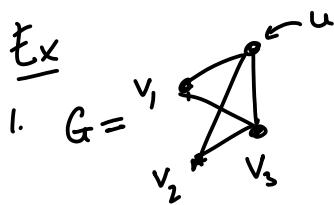

Prop

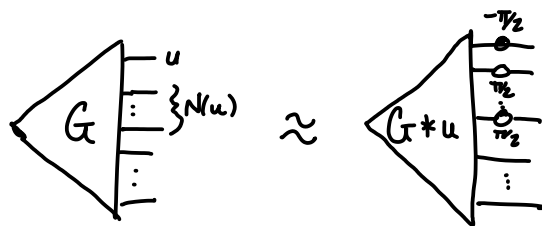


Graphically:

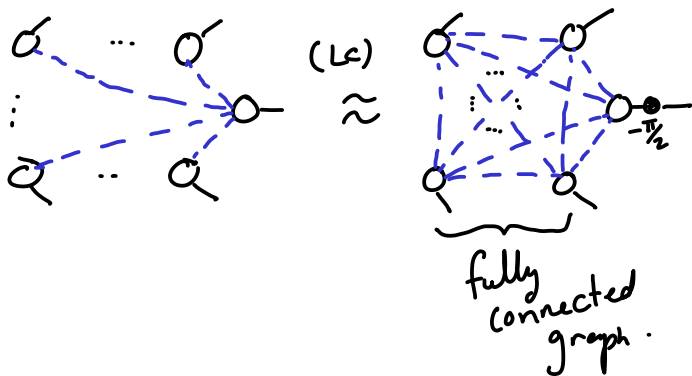


Q: Why is this the same as local comp?

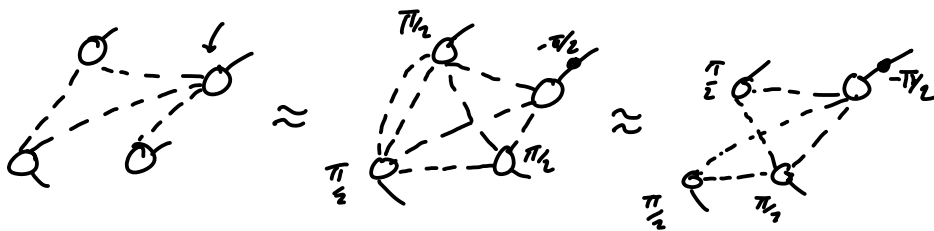A: Because $\alpha \dots \alpha \approx \alpha$





Prop

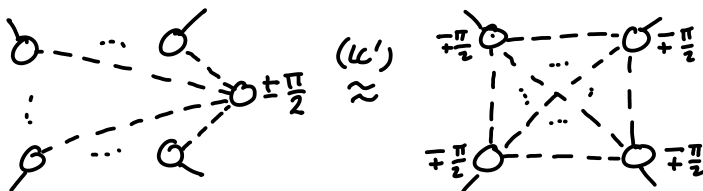

(*) $\frac{-\pi}{2} \approx \frac{\pi}{2}$
 (follows from
 EULER + CC)

Pf

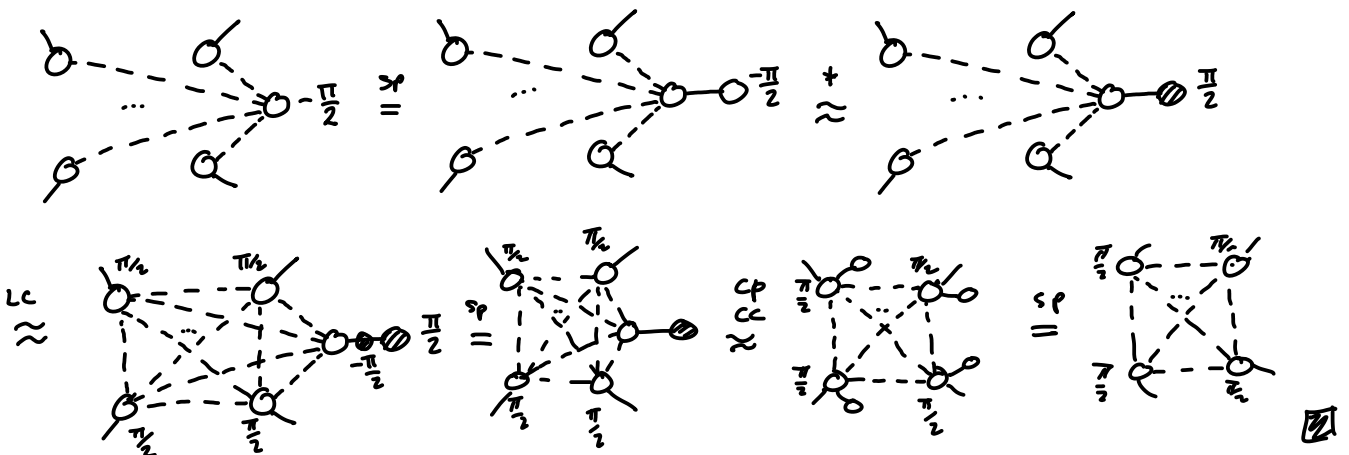

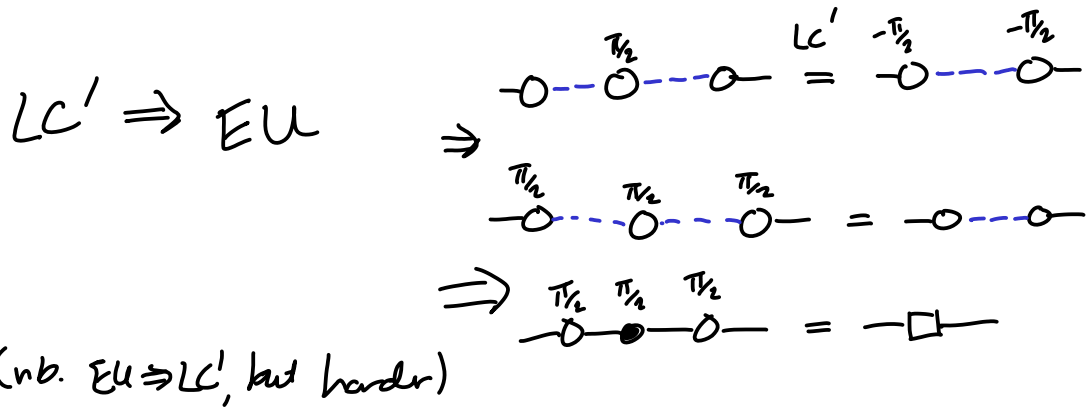

Pivoting.

Consider the (sc) rule:





add some context:




always deletes spiders!

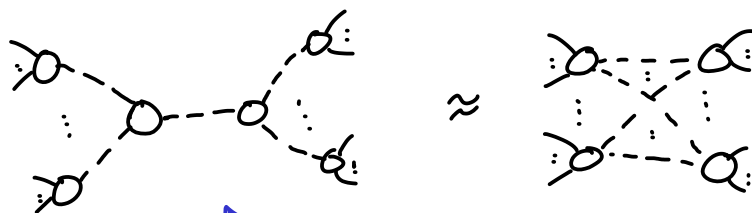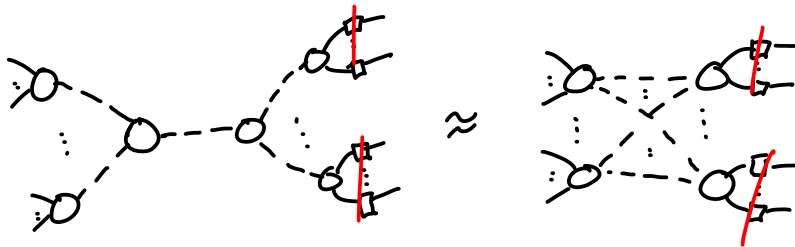Now, (cc) both sides to elim \times spiders:






deletes 2 adj. phase-free spiders.


Generalisation:

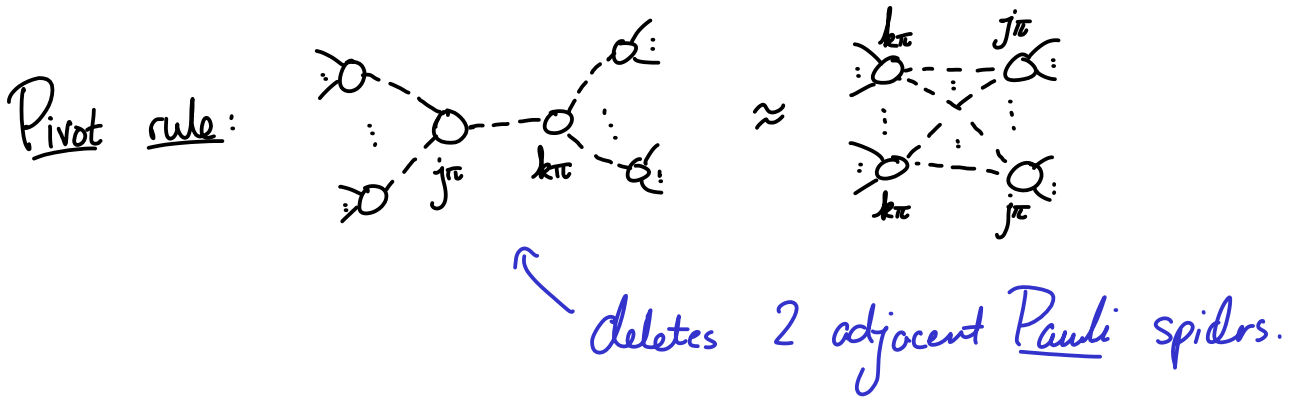

Q: What if they share neighbours?

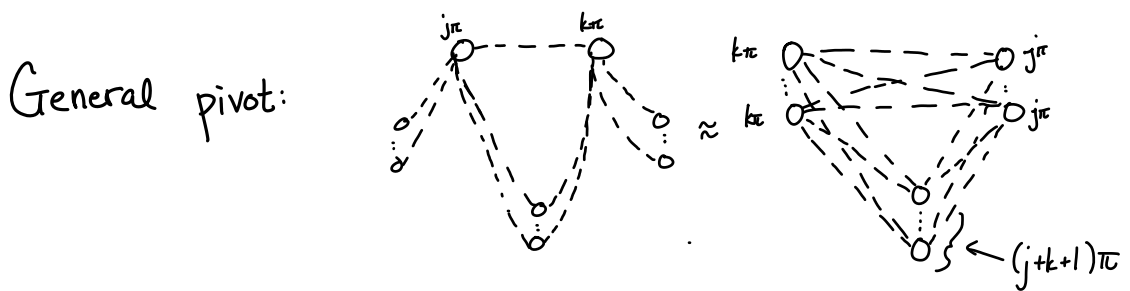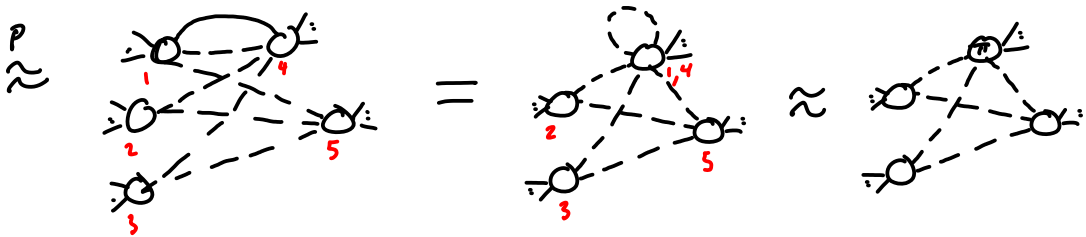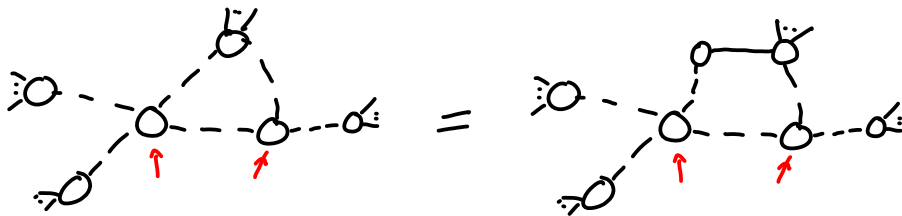

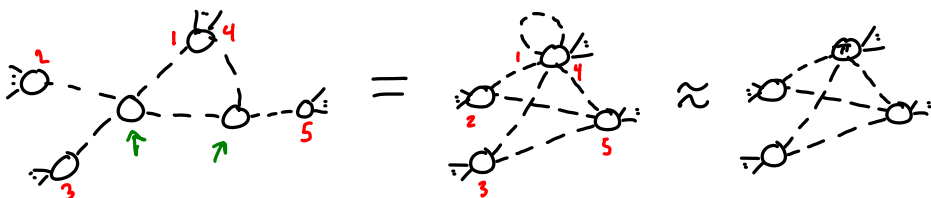Or, as I prefer to think about it, use the simpler rule, but allow boundary sp's to match twice:



Rewrite strategy (Clifford-simp.)

1. convert to a graph-like diagram
2. apply $LC' \times P'$ as long as possible.
3. remove isolated $\{0, \pi\}$ -spiders.

Prop 1 Clifford-simp terminates for any ZX-diag and removes all interior:

* $\pm \frac{\pi}{2}$ spiders

* pairs of connected $\{0, \pi\}$ -spiders

Recall: $m \text{ : } \boxed{\quad} \text{ : } n$ is a $2^n \times 2^m$ matrix.

$m=n=0 \Rightarrow 2^0 \times 2^0 = 1 \times 1$ matrix (a scalar)

Def A scalar ZX-diagram is a ZX-diag w/ no inputs and no outputs.

Cor (to Prop 1) There exists a terminating rewrite strategy that removes all spiders from a scalar Clifford diagram.

Pf First apply Clifford-simp. Then the only spiders left are 0 and π . For these:

$$0 \rightarrow 2 \cdot \begin{array}{c} \vdots \\ \vdots \\ \vdots \end{array}$$

$$\pi \text{ } 0 \rightarrow \emptyset$$

□

Q: What's left?

A: the scalar factor

$$\boxed{D_0} \rightarrow \lambda_1 \boxed{D_1} \rightarrow \lambda_2 \boxed{D_2} \rightarrow \dots \rightarrow \lambda_n \boxed{D_n} = \lambda_n \in \mathbb{C}$$

Application 1 (Efficient) strong simulation of Clifford circuits.

Problem For a circuit C , compute:


$$(*) \text{Prob}(x_1 \dots x_n | |\psi\rangle) \text{ where } |\psi\rangle = C|0 \dots 0\rangle.$$

... or more generally, for $k \leq n$, compute the marginal probability:

$$(**) \text{Prob}(x_1 \dots x_k | |\psi\rangle) = \sum_{x_{k+1}, \dots, x_n} \text{Prob}(x_1 \dots x_n | |\psi\rangle)$$

Born rule

$$\text{Prob}(x_1 \dots x_n | |\psi\rangle) := |\langle x_1 \dots x_n | C|0 \dots 0\rangle|^2$$

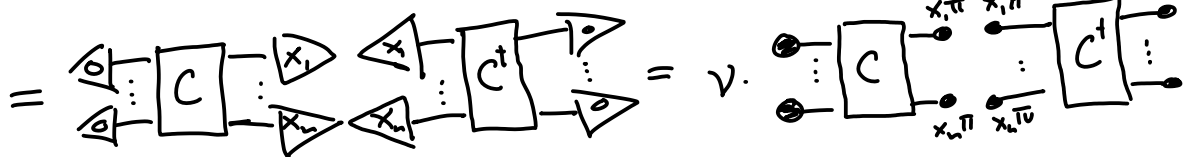

$$\Rightarrow \text{Prob}(x_1 \dots x_k | |\psi\rangle) = \sum_{x_{k+1}, \dots, x_n} \text{Prob}(x_1 \dots x_n | |\psi\rangle) = v'$$

$$\left(\sum_x \overset{x\pi}{\bullet} \overset{x\pi}{\bullet} = 2 \cdot \sum_x |x\rangle\langle x| = 2I \right)$$

\curvearrowright ZX-diagram of (**)

Algorithm 1: For a circuit C :

1. Let D be the ZX-diagram of $\text{Prob}(x_1, \dots, x_k | C | 0 \dots 0)$.
2. Apply Clifford-simp to get a number.

Prop 1 Algorithm 1 terminates in polynomial time (in the # of qubits or gates of C).

Pf Assume basic diagram operations (add/remove spider/wire) take constant time. If C has n qubits & k gates, D has at most $S := 2 \cdot (2n + 2k) = 4(n+k)$ spiders. Then:

— Each rewrite removes 1 or 2 spiders, so there are at most $4(n+k)$ steps.

— Each step adds/removes at most $(4(n+k))^2$ edges, so Algorithm 1 performs $O((n+k)^3)$ basic graph operations. \square

Rem this is not optimal. A good choice of LC' and P' steps actually takes $O(n^2k)$ time; \Rightarrow if $k \gg n$, this makes a big difference!

IDEA:

1. Avoid big spiders: $\begin{array}{c} \alpha \\ \circ \end{array} - \begin{array}{c} \beta \\ \circ \end{array} \rightarrow \begin{array}{c} \alpha+\beta \\ \circ \end{array}$ ~~$\begin{array}{c} \alpha \\ \circ \end{array} - \begin{array}{c} \beta \\ \circ \end{array}$~~ $\begin{array}{c} \alpha \\ \circ \end{array} - \begin{array}{c} \beta \\ \circ \end{array}$

2. Apply LC' & P' from left-to-right:



\Rightarrow each step involves at most $O(n)$ spiders (hence $O(n^2)$ wires)

Lecture 12

Def A graph-like ZX-diagram is in AP-form if all interior spiders:

- have phase $\in 0, \pi$
- are only connected to boundary spiders.


Def A ZX-diagram is in graph-state w/ local Clifford (GSLC) form if it has

- * all Z spiders, fused as much as possible
- * all spiders are connected to exactly 1 input (possibly via a 1-qubit Clifford unitary)


AP \rightarrow GSLC:

2 cases:

CASE 1:

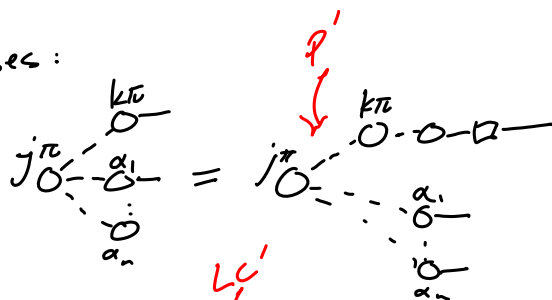

CASE 2:

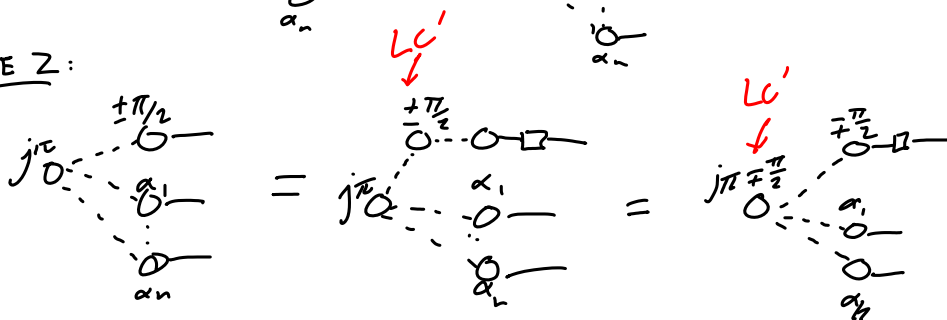


Application 2 Efficient synthesis of Clifford circuits.

Clifford diagram \rightarrow AP-form \rightarrow GSLC


- * only internal spiders are ~~Z~~
- * no internal spiders.

Algorithm 2 (Clifford n -synthesis)

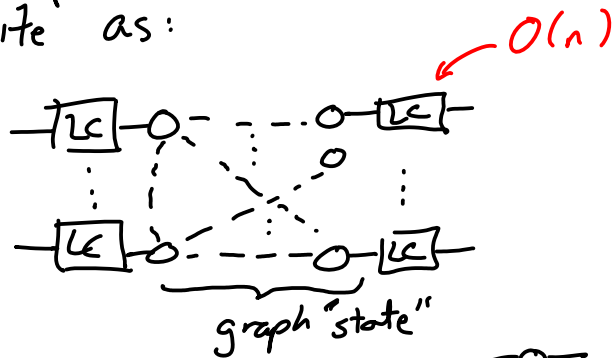
1. For an n -qubit Clifford circuit C , translate to ZX-diagram D .
2. Compute GSLC form.
3. Write as:




4. unfuse CZ gates =  and

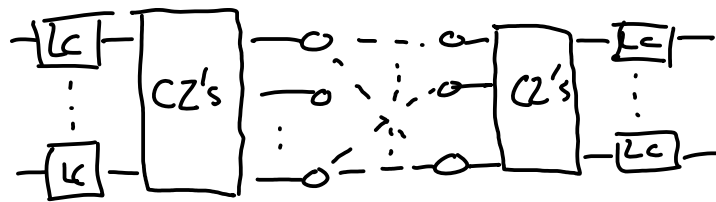

3. colour-change:

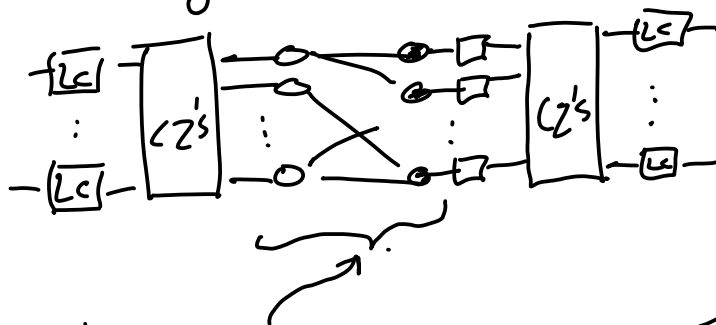

4. extract parity map as CNOTs

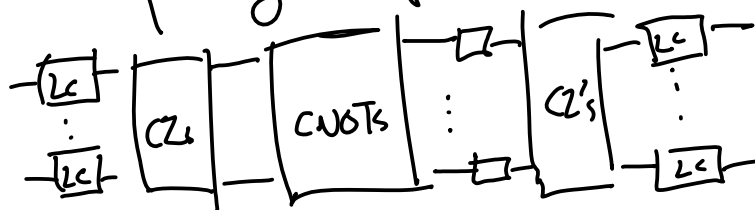


Prop Any Clifford circuit can be written w/ at most $O(n^2)$ gates!

APPLICATION 3 Completeness of the ZX-calculus for Clifford diagrams.


Thm (COMPLETENESS) For Clifford ZX-diagrams D_1, D_2 ,
 if $D_1 \equiv D_2$ then $D_1 \stackrel{ZX}{=} D_2$.
 (matrices are equal) (can (efficiently!) transform D_1 to D_2 with the ZX-calc.)

IDEA: Look at the AP form.

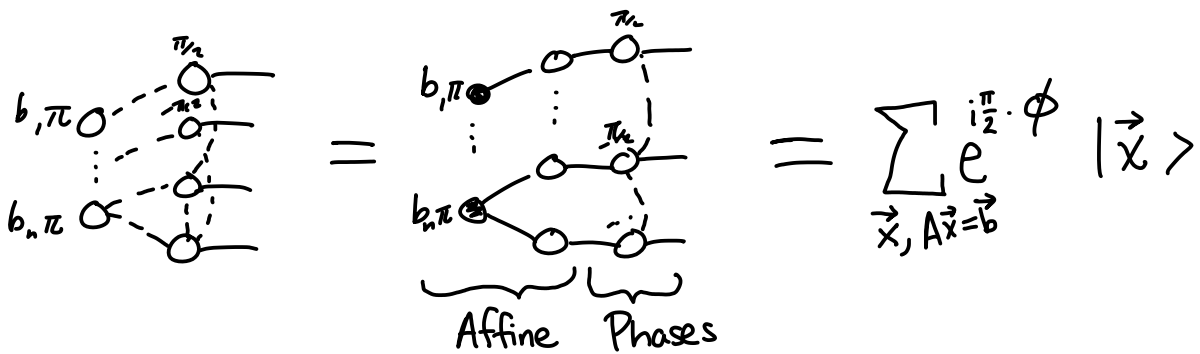Def A graph-like ZX-diagram is in AP-form if all interior spiders:
 - have phase $\in 0, \pi$
 - are only connected to boundary spiders.



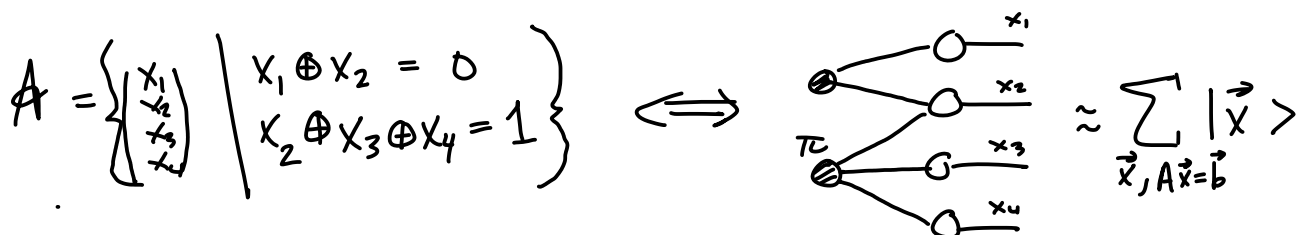$A = \{ \vec{x} \mid A\vec{x} = \vec{b} \}$ is an affine subspace of \mathbb{F}_2^n .
 := a solution to a set of linear eqns, e.g:



ϕ is a phase polynomial

$$\begin{array}{c} \text{---} \pi/2 \\ \text{---} \text{---} \\ \text{---} \end{array} = e^{i\pi \cdot (\frac{1}{2}x)} |x\rangle$$


$$\begin{array}{c} \text{---} -\pi/2 \\ \text{---} \text{---} \\ \text{---} \end{array} = e^{i\pi \cdot (-\frac{1}{2}x)} |x\rangle$$

$$\begin{array}{c} \text{---} \pi/2 \\ \text{---} \text{---} \\ \text{---} \end{array} = (-1)^{x_1 x_2} \begin{array}{c} \text{---} x_1 \\ \text{---} x_2 \end{array} = e^{i\pi(x_1 x_2)} \begin{array}{c} \text{---} x_1 \\ \text{---} x_2 \end{array}$$

Phase Polynomial

$$\begin{array}{c} \text{---} \pi/2 \\ \text{---} \text{---} \\ \text{---} \end{array} = e^{i\pi(x_1 x_2)} \quad \begin{array}{c} \text{---} \pi/2 \\ \text{---} \text{---} \\ \text{---} \end{array} = e^{i\pi(x_1 x_2)} e^{i\pi(\frac{1}{2}x_1)} \quad \begin{array}{c} \text{---} \pi/2 \\ \text{---} \text{---} \\ \text{---} \end{array} = e^{i\pi(x_1 x_2 + \frac{1}{2}x_1)} \begin{array}{c} \text{---} x_1 \\ \text{---} x_2 \end{array}$$

$$U|\vec{x}\rangle = e^{i\pi \cdot \phi} |\vec{x}\rangle \quad \text{where } \phi = \frac{1}{2}x_1 - \frac{1}{2}x_3 + x_2 + x_3 x_4$$

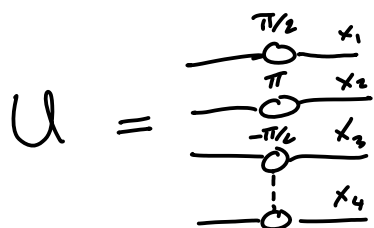

Def An AP-form is in reduced AP-form if it is \emptyset or A is in reduced echelon form and the polynomial ϕ only contains free variables from A .

$$\begin{array}{c} b_1 \\ \vdots \\ b_k \end{array} \begin{array}{c} \text{---} \pi/2 \\ \text{---} \pi/2 \\ \text{---} \pi/2 \\ \text{---} \pi/2 \end{array} = \sum_{\vec{x}, A\vec{x}=\vec{b}} e^{i\pi \cdot \phi} |\vec{x}\rangle \quad A = \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{pmatrix}$$

Free var x_3
Echelon form

PROP Reduced AP-form is unique.


PF (Linear algebra)

PROP For Clifford diag D , $D \stackrel{zx}{=} D'$ \leftarrow reduced AP-form.
PF (zx can do Gaussian elimination!)

COR Completeness!

CNOT + phase Circuits


(non-Clifford)

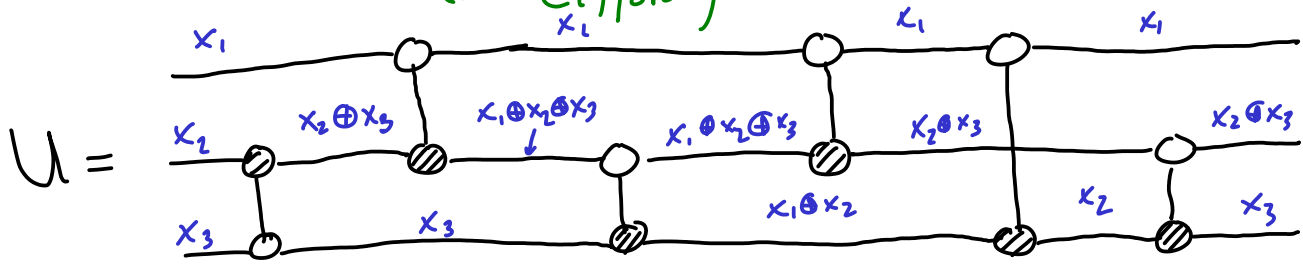

$$U |x_1, x_2, x_3\rangle = |x_1, x_2 \oplus x_3, x_3\rangle$$

Q: What happens when we add phase gates?

$$Z[\alpha] :: |x\rangle \mapsto e^{i\alpha \cdot x} |x\rangle$$

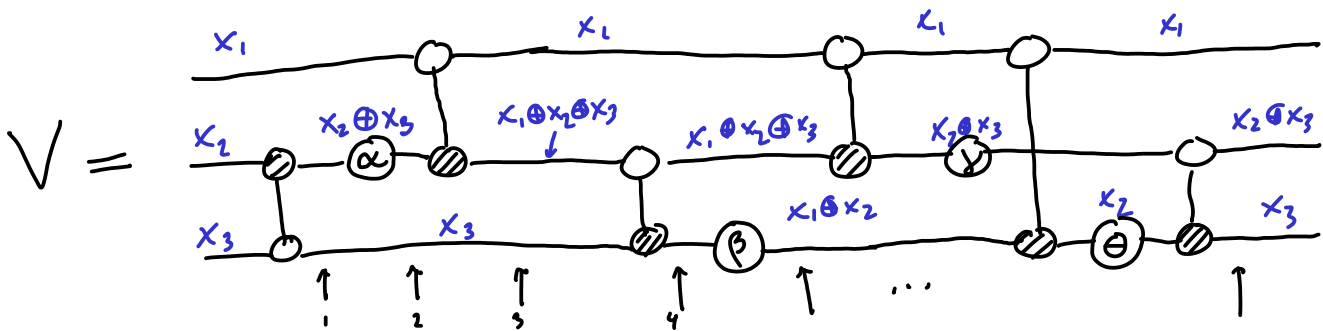

$$|x_1, x_2, x_3\rangle \mapsto |x_1, x_2 \oplus x_3, x_3\rangle$$

$$\mapsto e^{i\alpha \cdot (x_2 \oplus x_3)} |x_1, x_2 \oplus x_3, x_3\rangle$$

$$\mapsto e^{i\alpha(x_2 \oplus x_3)} |x_1, x_1 \oplus x_2 \oplus x_3, x_3\rangle$$

$$\mapsto e^{i\alpha \cdot (x_2 \oplus x_3)} |x_1, x_1 \oplus x_2 \oplus x_3, x_1 \oplus x_2\rangle$$

$$\mapsto e^{i[\alpha \cdot (x_2 \oplus x_3) + \beta \cdot (x_1 \oplus x_2)]} |x_1, x_1 \oplus x_2 \oplus x_3, x_1 \oplus x_2\rangle$$

$\mapsto \dots$

$$\mapsto e^{i[\alpha \cdot (x_2 \oplus x_3) + \beta \cdot (x_1 \oplus x_2) + \gamma \cdot (x_2 \oplus x_3) + \theta \cdot x_2]} |x_1, x_2 \oplus x_3, x_3\rangle$$

Prop Any CNOT+phase circuit describes a unitary of the form:

$$U :: |\vec{x}\rangle \mapsto e^{i\phi(\vec{x})} |L\vec{x}\rangle$$

↑ phase polynomial
↑ parity matrix.


From the example above: $L = \begin{pmatrix} 1 & 0 & 0 \\ 0 & 1 & 1 \\ 0 & 0 & 1 \end{pmatrix}$ and

$$\phi(x_1, x_2, x_3) = (\alpha + \gamma) \cdot (x_2 \oplus x_3) + \beta \cdot (x_1 \oplus x_2) + \theta \cdot x_2$$

↑ phase-folding

Q: can we re-synthesise a circuit for (L, ϕ) ?

For L , we have:

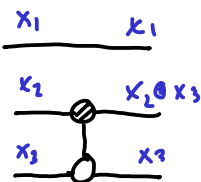

To get ϕ , we need to place Z-phases on wires labelled: $x_2 \oplus x_3$, $x_1 \oplus x_2$, and x_2

Only $x_1 \oplus x_2$ is missing, so lets (temporarily) create it:

